

GATE SOLUTIONS
ELECTRONICS & COMMUNICATION
ENGINEERING

1987-2020



Office: F-126, (Lower Basement), Katwaria Sarai, New Delhi-110 016

Phone: 011-26522064 ■ **Mobile:** 81309 09220, 97118 53908

Email: info.publications@iesmaster.org, info@iesmaster.org

Web: iesmasterpublications.com, iesmaster.org



IES MASTER PUBLICATION

F-126, (Lower Basement), Katwaria Sarai, New Delhi-110016

Phone : 011-26522064, **Mobile** : 8130909220, 9711853908

E-mail : info.publications@iesmaster.org

Web : iesmasterpublications.com

All rights reserved.

Copyright © 2020, by IES MASTER Publication. No part of this booklet may be reproduced, or distributed in any form or by any means, electronic, mechanical, photocopying, recording, or otherwise or stored in a database or retrieval system without the prior permission of IES MASTER Publication, New Delhi. Violates are liable to be legally prosecuted.

First Edition : 2016

Second Edition : 2017

Third Edition : 2018

Fourth Edition : 2019

Fifth Edition : 2020

PREFACE

The Graduate Aptitude Test in Engineering (GATE) is an All-India examination administered and conducted in eight zones across the country by the GATE Committee comprising of Faculty members from IISc, Bangalore and other seven IITs on behalf of the National Coordinating Board, Department of Education, Ministry of Human Resources Development.

The GATE score/rank is used for admissions to Post Graduate Programmes (ME, M.Tech, MS, direct PhD) in institutes like IIT and IISc, etc. with financial assistance offered by the Ministry of Human Resource Development. PSUs too use the GATE scores for recruiting candidates for various prestigious jobs with attractive remuneration.

The door to GATE exam is through previous year question papers. If you are able to solve question papers in access of 10 years, you are sure to clear the GATE exam, and open new vistas of career and learning.

The **Electronics & Communication Engineering GATE 2021** book from IES Master offers detailed topic-wise solutions for the past 34 years question papers. The emphasis is clearly on the understanding of concepts and building upon a holistic picture. So as you finish a topic, for instance, Basics of Network Analysis, you will find all the previous years' question papers with detailed explanation under that particular topic.


The approach has been to provide explanation in such a way that just by going through the solutions, students will be able to understand the basic concepts and will apply these concepts in solving other questions that might be asked in future exams.

Every care has been taken to bring an error-free book. However, comments, suggestions, and feedback for improvement in the future editions are most welcome.

**IES Master Publication
New Delhi**

CONTENT

1. Network Theory	1 – 117
2. Signal and Systems	118 – 215
3. Electronic Devices	216 – 292
4. Analog Electronics	293 – 421
5. Digital Circuits	422 – 521
6. Microprocessor	522 – 545
7. Control Systems	546 – 662
8. Communications	663 – 791
9. Electromagnetics	792 – 916
10. Mathematics	917 – 978
11. General Aptitude	979 – 1018

 

UNIT-1

NETWORK THEORY

SYLLABUS

Network solution methods : nodal and mesh analysis; Network theorem; superposition, Thevenin and Norton's, maximum power transfer; Wye-Delta transformation; Steady state sinusoidal analysis using phasors; Time domain analysis of simple linear circuits; solution of network equations using Laplace transform; Frequency domain analysis of RLC circuits; Linear 2-port network parameters: driving point and transfer functions; State equations for network

CONTENTS

Chapter No.	Topic	Page No.
1.	Basics of Network Analysis	02–22
2.	DC Transients and Steady State Response	23–64
3.	Resonance	65–72
4.	Network Theorems	73–91
5.	Two Port Networks	92–109
6.	Network Functions and Network Synthesis	110–114
7.	Network Graphs	115–117

1


BASICS OF NETWORK ANALYSIS

1- Mark

1. A connection is made consisting of resistance A in series with a parallel combination of resistances B and C. Three resistors of the value 10Ω , 5Ω , 2Ω are provided. Consider all possible permutations of the given resistors into the positions A, B, C, and identify the configurations with maximum possible overall resistance, and also the ones with minimum possible overall resistance. The ratio of maximum to minimum value of the resistances (upto second decimal place) is _____


[GATE-2017]

 2. In the network shown in the figure, all resistors are identical with $R = 300\Omega$. The resistance R_{ab} (in Ω) of the network is _____.



[GATE-2015]

 3. In the given circuit, the values of V_1 and V_2 respectively are




- (a) 5V, 25V (b) 10V, 30V
(c) 15V, 35V (d) 0V, 20V

[GATE-2015]

 4. In the circuit shown, the switch SW is thrown from position A to position B at time $t = 0$. The energy (in μJ) taken from the 3V source to


charge the $0.1\mu\text{F}$ capacitor from 0V to 3V is



- (a) 0.3 (b) 0.45
(c) 0.9 (d) 3


[GATE-2015]

 5. In the circuit shown, the average value of the voltage V_{ab} (in Volts) in steady state condition is _____




[GATE-2015]

 6. At very high frequencies, the peak output voltage V_0 (in Volts) is _____



[GATE-2015]

 7. In the circuit shown, the voltage V_x (in Volts) is _____



[GATE-2015]

- (a) -105 V
- (b) +105 V
- (c) - 15 V
- (d) + 15 V


[GATE-1993]

- (a) 0 A
- (b) 4 A
- (c) 1 A
- (d) None of the above

[GATE-1997]


3- Marks

 1. In the circuit shown, the current i_D through the ideal diode (zero cut in voltage and zero forward resistance) equals



5- Marks

 1. Find the input resistance R_{in} of the infinite section resistive network shown in figure.



[GATE-1996]

ANSWER KEY

1 Mark

- 1. (2.14)
- 2. (100)
- 3. (a)
- 4. (c)
- 5. (5)
- 6. (0.5)
- 7. (8)
- 8. (2.8)
- 9. (a)
- 10. (0.5)
- 11. (c)
- 12. (b)
- 13. (b)
- 14. (a)
- 15. (c)
- 16. (a)

- 17. (d)
- 18. (a)
- 19. (c)
- 20. (a)
- 21. (d)
- 22. (a)
- 23. (b)
- 24. (c)
- 25. (b)
- 26. (a)
- 27. (d)
- 28. (a)
- 29. (d)
- 30. (a & d)

2 Marks

- 1. (8.00)
- 2. (a)

- 3. (1)
- 4. (d)
- 5. (5)
- 6. (-1A)
- 7. (1.5)
- 8. (20)
- 9. (29.09)
- 10. (2.504)
- 11. (10)
- 12. (0.4083)
- 13. (2.618)
- 14. (c)
- 15. (d)
- 16. (c)
- 17. (a)
- 18. (a)
- 19. (c)

- 20. (b)
- 21. (a)
- 22. (None of these)
- 23. (d)
- 24. (d)
- 25. (d)
- 26. (d)
- 27. (b)
- 28. (b)
- 29. (d)
- 30. (a)


3 Marks

- 1. (c)

EXPLANATIONS

1- Mark

Sol-1: (2.14)

 

Resistor are 2, 5 and 10Ω

For maximum resistance B = 2, C = 5, A = 10

$$R_{\max} = \frac{80}{7}$$


for minimum resistance,

A = 2, B = 5, C = 10

$$R_{\min} = \frac{16}{3}$$

$$\frac{R_{\max}}{R_{\min}} = \frac{(80/7)}{(16/3)} = 2.14$$

Sol-2: (100)

 


[Here, branch 'pqrs' is removed as no current flows through it, because it forms a balanced bridge]

$$\therefore R_{\text{eq}} = (2R) \parallel (2R) \parallel R \parallel R$$

$$= R \parallel R \parallel R = \frac{R}{3} = 100\Omega$$

Sol-3: (a)

 

Applying nodal analysis at node (1), we get

$$5 = \frac{x}{4} + \frac{x}{4} + 2I$$

$$\Rightarrow 5 = \frac{2x}{4} + 2 \times \frac{x}{4} \quad [\because x = 4I]$$

$$\therefore x = 5$$

$$\text{Now, } V_1 = 5V \quad [\because x = V_1]$$


$$V_1 + 5 \times 4 - V_2 = 0$$

[KVL in the outermost loop]

$$\Rightarrow V_2 = 5 + 5 \times 4 = 25V$$

Sol-4: (c)

 Initially capacitor is uncharged. For $t > 0$, the circuit will be :



Current in RC circuit while charging is given by :

$$i(t) = \frac{V_0}{R} e^{-t/RC} \text{ where } V_0 = 3V$$

$$\text{Power delivered by the source} = P = 3i(t) \quad [\because P = V.I]$$

$$\text{Also, Energy} = \int_0^t P dt = \int_0^t 3i(t) dt$$

Capacitor gets fully charged at steady state i.e $t = \infty$.

$$\begin{aligned} \therefore E &= \int_0^{\infty} 3 \cdot \frac{V_0}{R} e^{-t/RC} dt \\ &= \frac{3V_0}{R} \times \frac{(-1)}{(1/RC)} [e^{-t/RC}]_0^{\infty} \end{aligned}$$